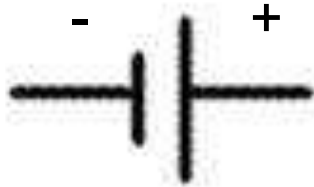


Electronic circuit analysis




Switch



Voltage Source



bulb

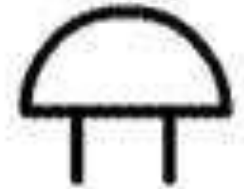

bell



electromotor



amperemeter



voltmeter



Resistor


1 Ohm's law

2 Kirchhoff's theorem

3 Thevenin-Norton theorem


1 Ohm's law

$$V = I \cdot R$$

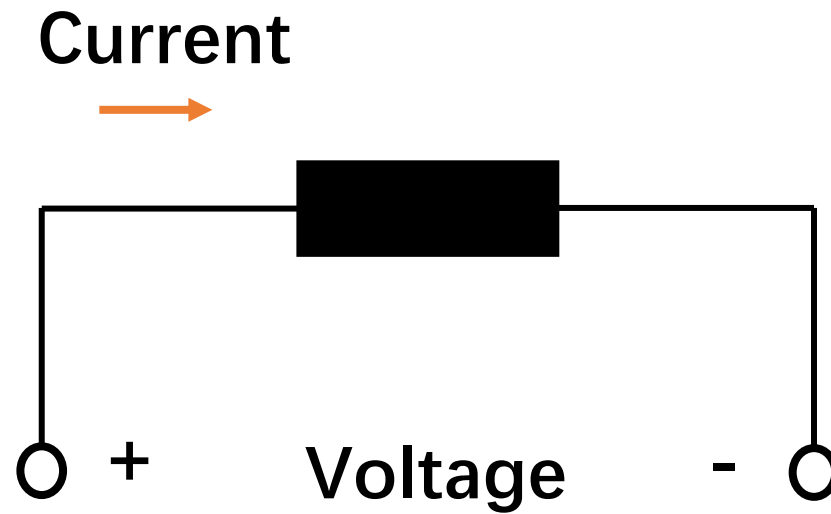

How it works?

Equivalent 等效

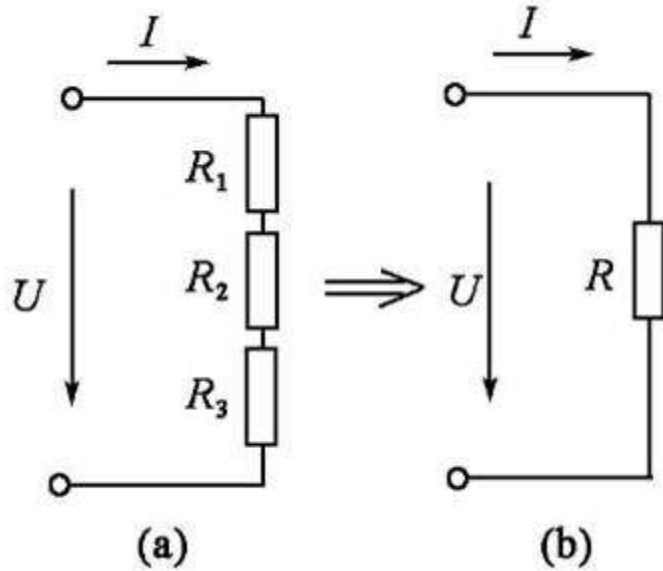

Series resistor
Equivalent

$$R = R_1 + R_2 + R_3$$


Only one current in the circuit, but

$$U = U_1 + U_2 + U_3$$

$$U_i = R_i / R$$

The partial voltage of a resistor in a circuit depends on the ratio of its resistance to the total resistance.

circuit branch 支路

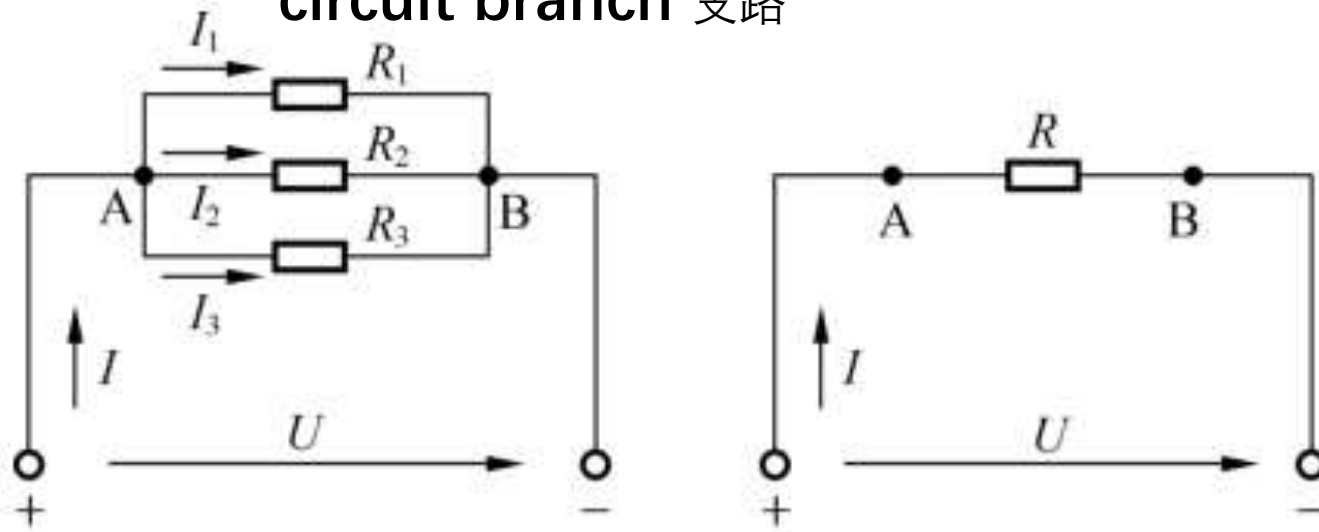

Parallel resistor
Equivalent

As a result, $U=U_1=U_2=U_3$

$$I=I_1+I_2+I_3$$

$$I_i=?$$

并联电路的总电阻


$$R = \frac{U}{I} = \frac{U}{I_1 + I_2 + \dots + I_n}$$

$$\therefore \frac{1}{R} = \frac{I_1 + I_2 + \dots + I_n}{U}$$

$$= \frac{I_1}{U} + \frac{I_2}{U} + \dots + \frac{I_n}{U}$$

$$= \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$
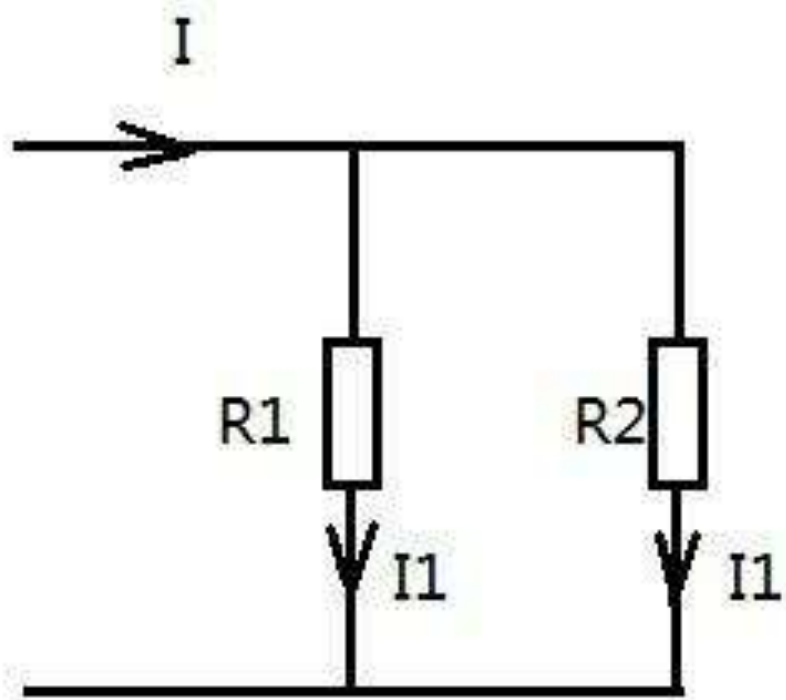
$$\therefore \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$




$$I_1 = \frac{R_2}{R_1 + R_2} I$$

$$I_2 = \frac{R_1}{R_1 + R_2} I$$

Branch shunt law

Application

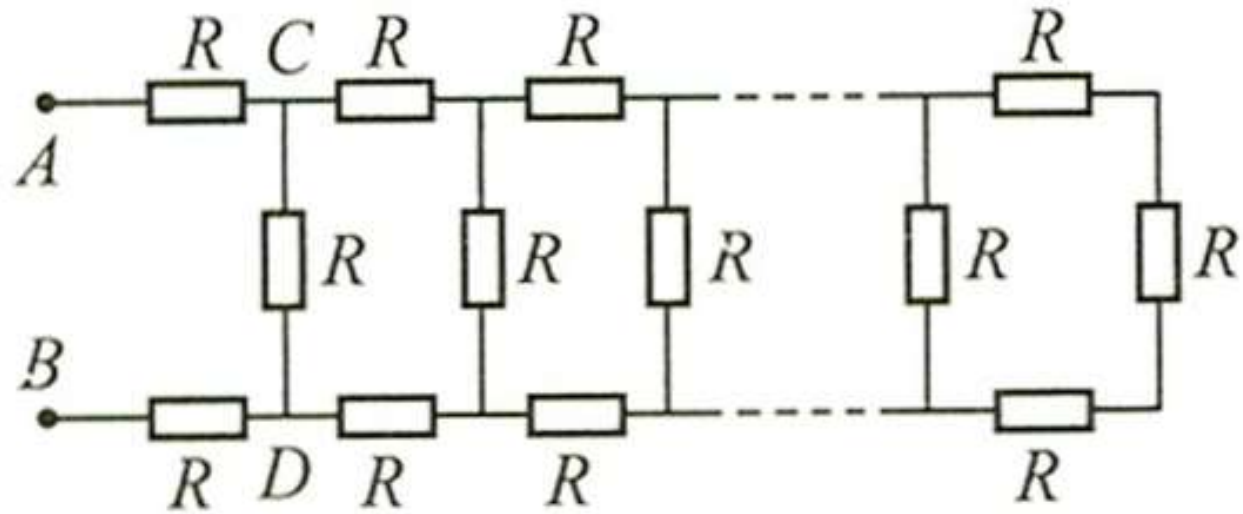


Infinite resistance network


$$R_{AB} = R_{CD}$$







Application

Equivalent transformation

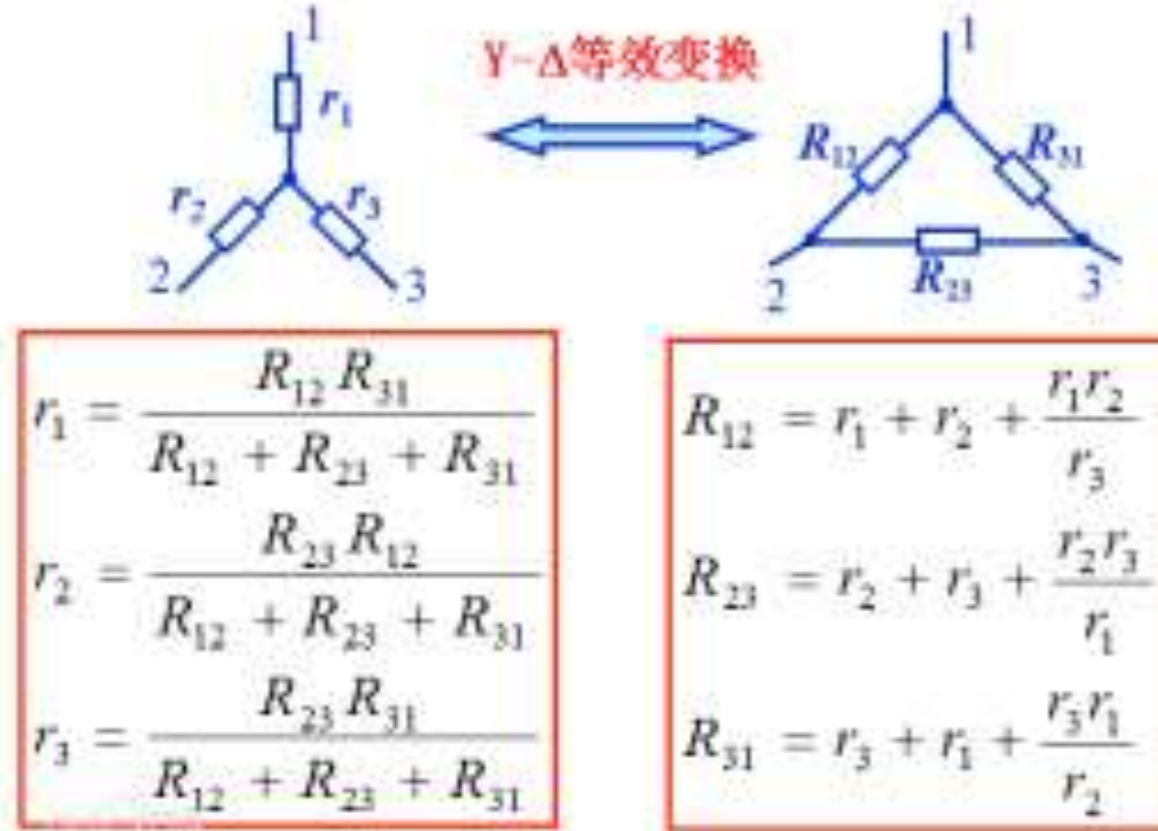


Complex resistance network

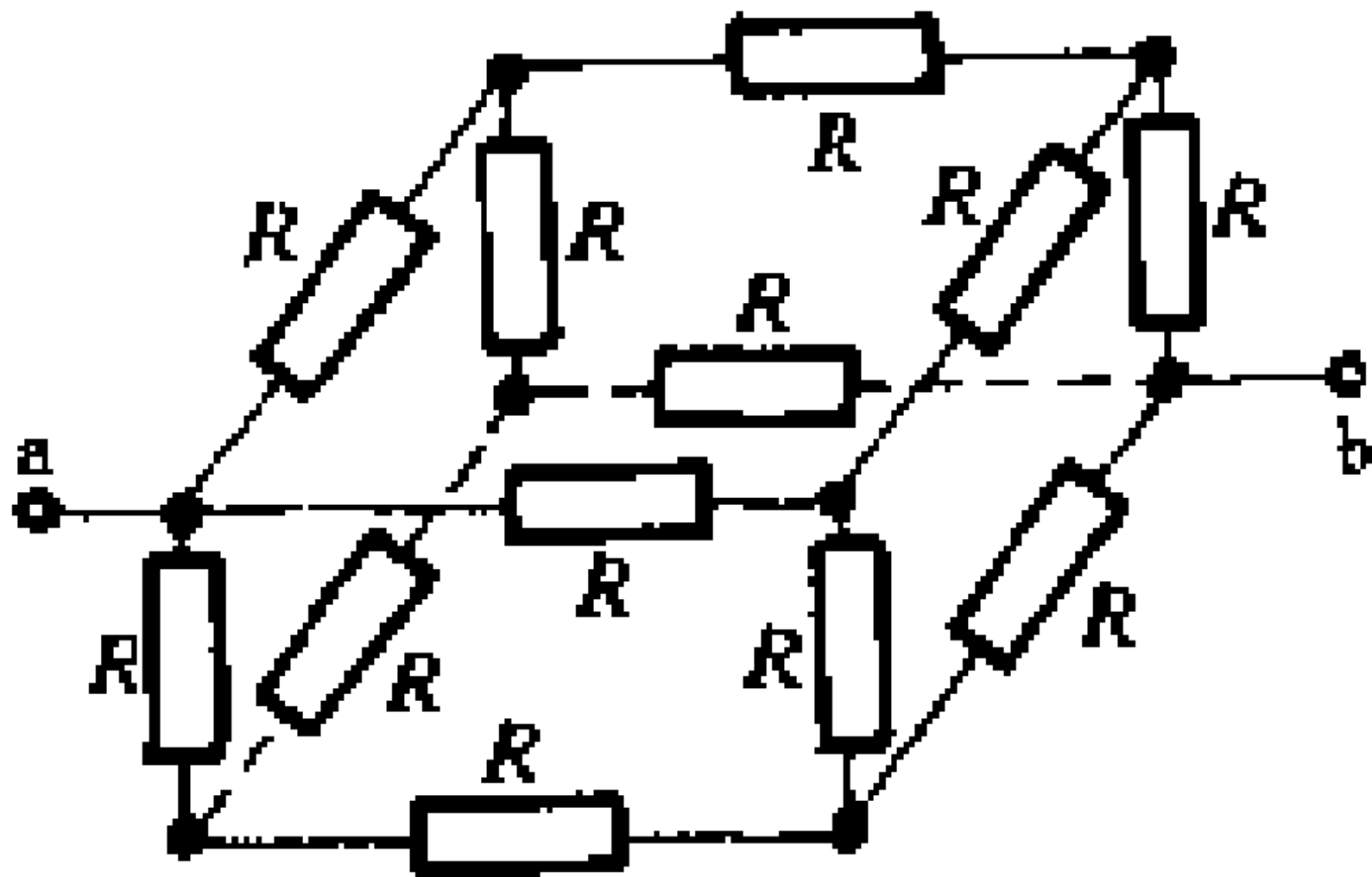

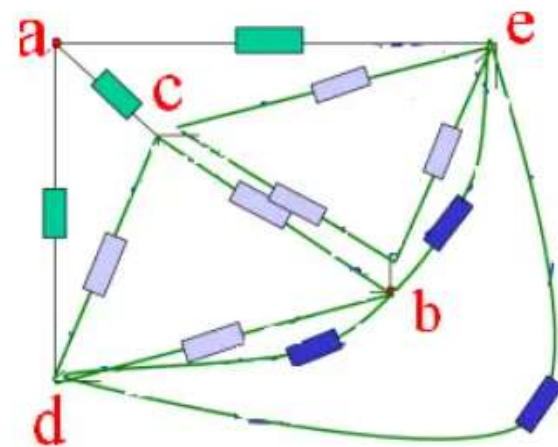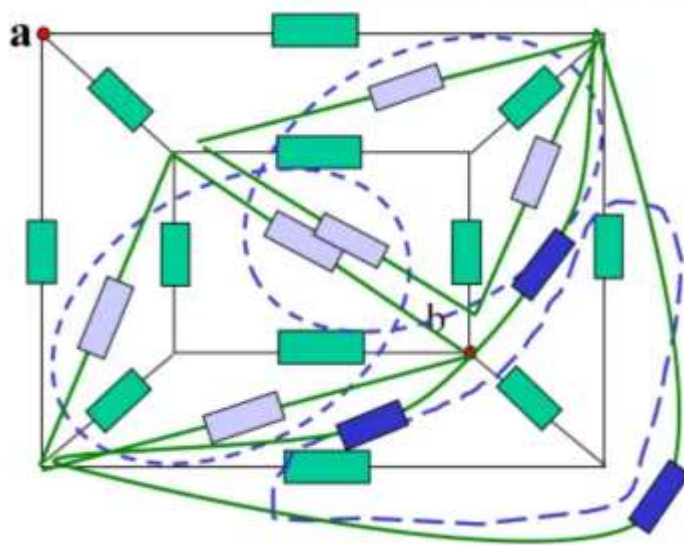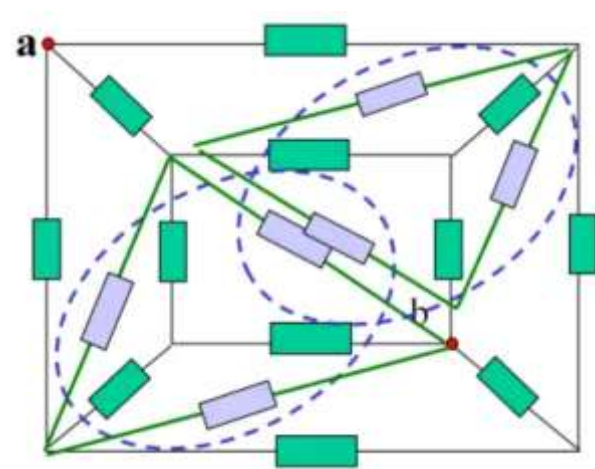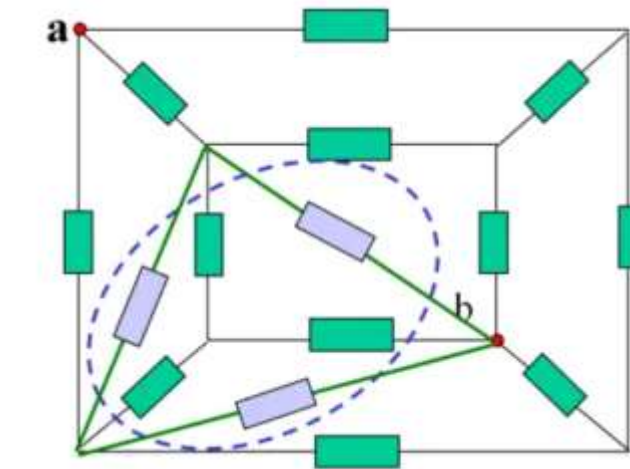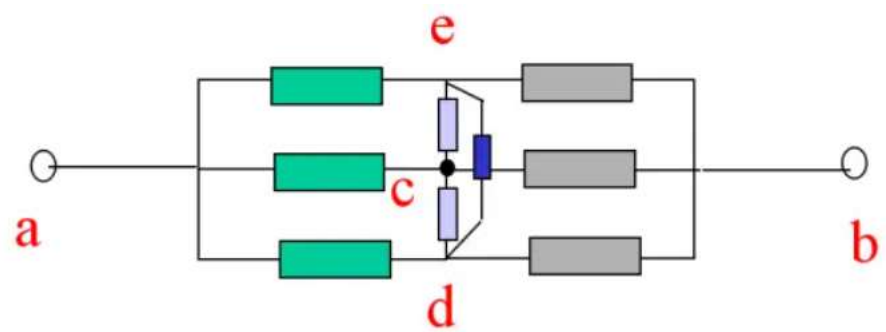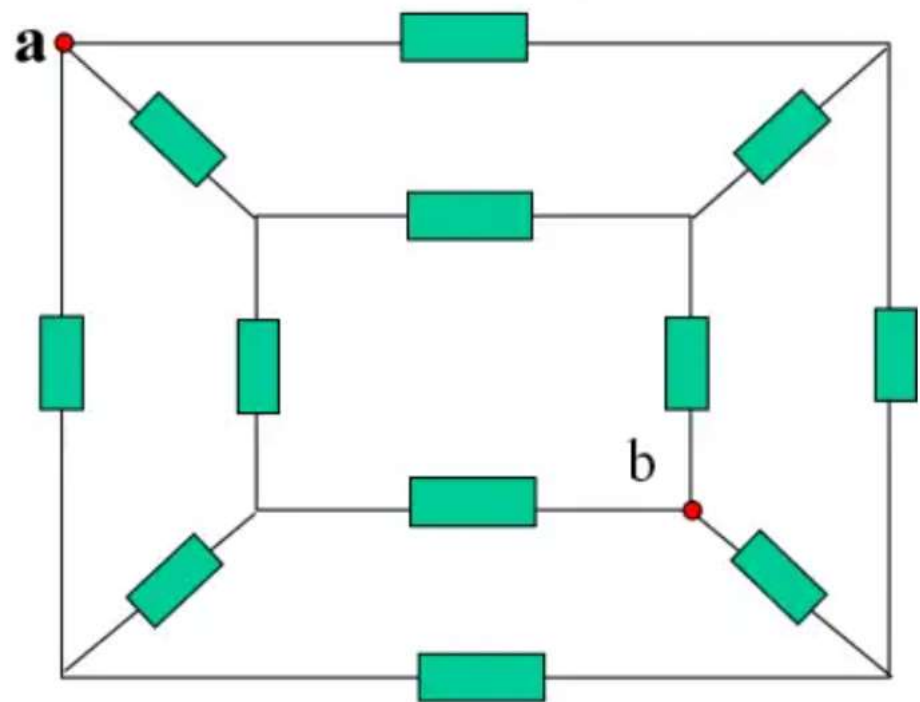

Application

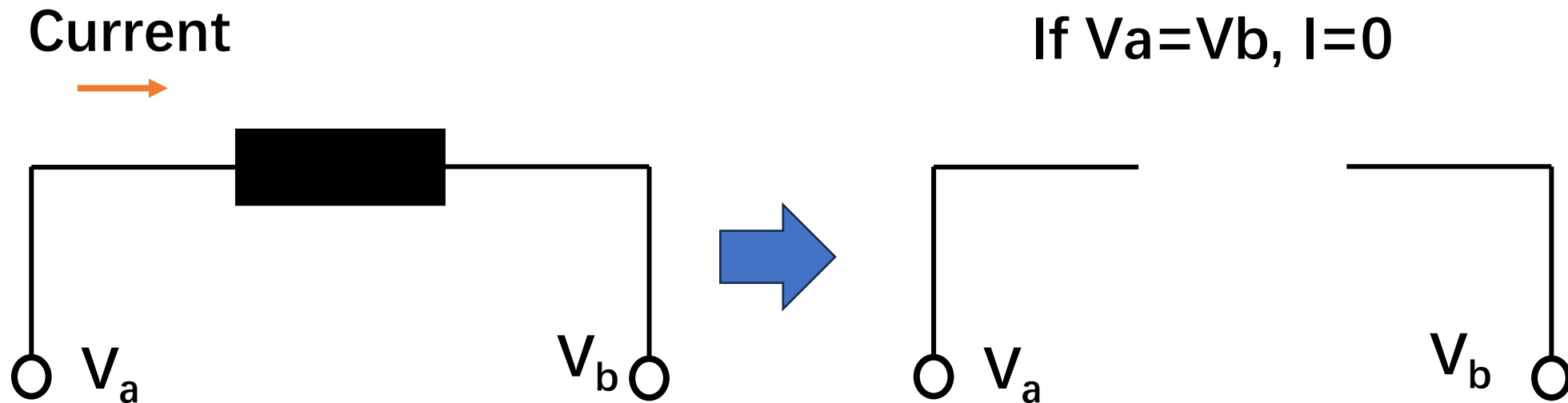
Equivalent Principle: When the potential between two points is equal, No circuit will be generated between the two points, equivalent to disconnection!




Equipotential point :

These equipotential points play a very important role in the circuit. According to Ohm's theorem, we can find them from the geometric symmetry of the circuit.

For example, try analysis again

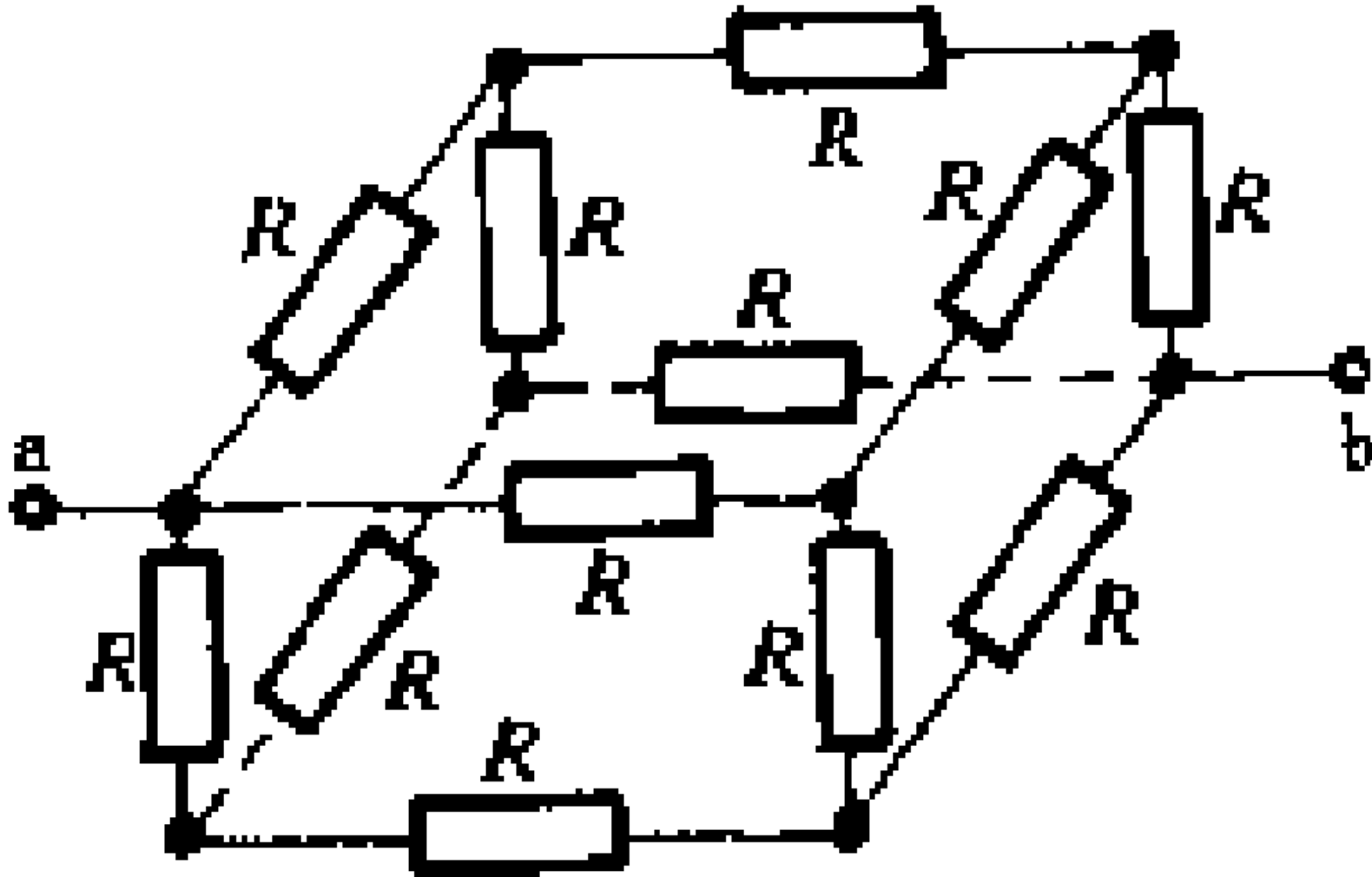

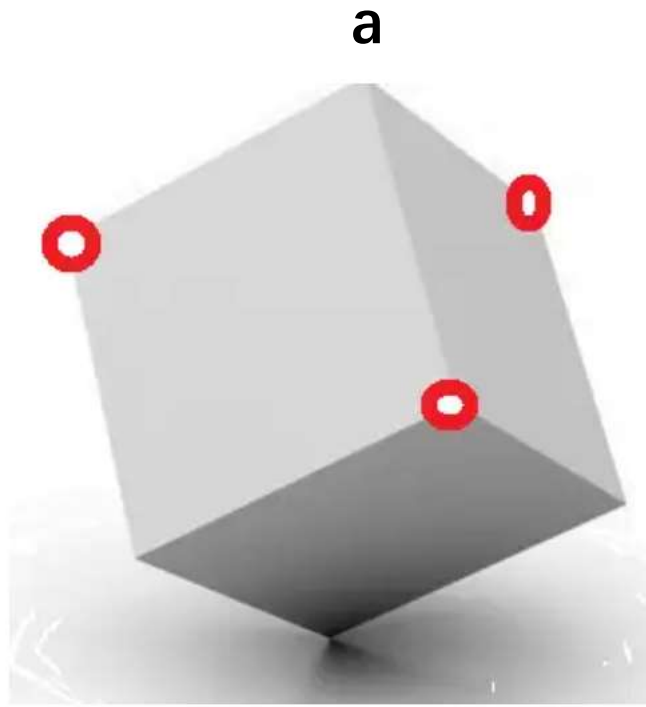


1 Find symmetry points

2 Find circuit branches

3 Use Equivalent Principle

b

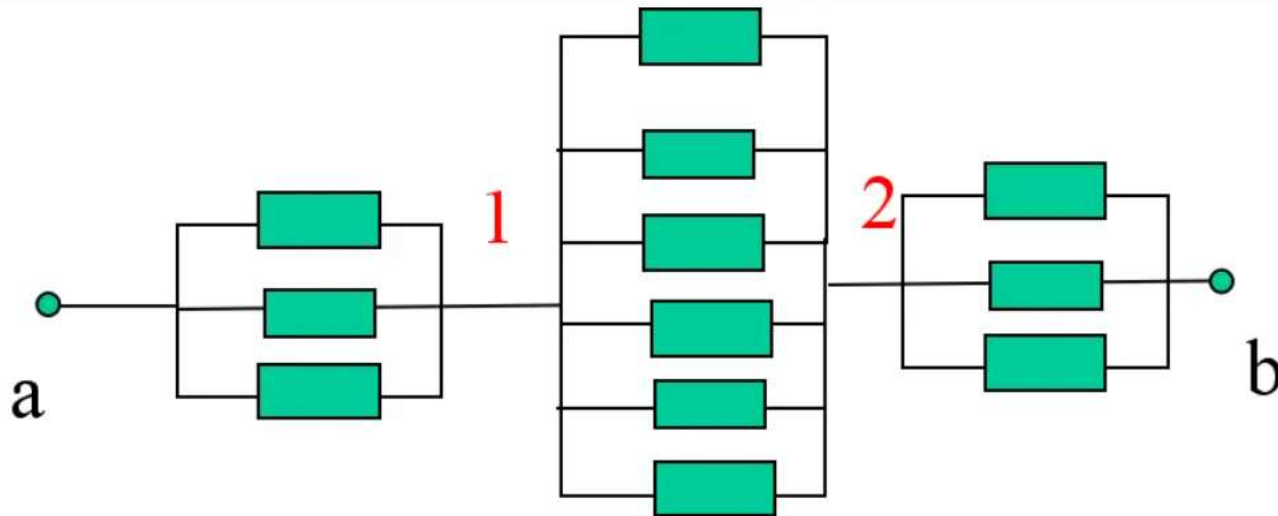

$$R_{ab} = R/3 + R/6 + R/3 = 5R/6$$

Conclusion:

$$U_i = R_i / R$$

Voltage division theorem of series circuit

$$I_1 = \frac{R_2}{R_1 + R_2} I$$

Branch shunt law

& Equivalent Principles

Proof of om's law




2 Kirchhoff's law

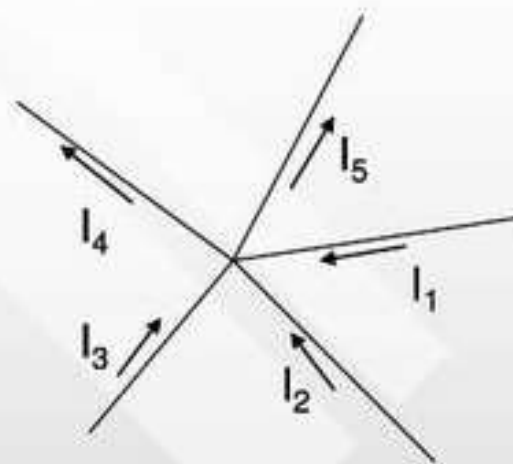1. 基尔霍夫电流定律 (KCL)

$$\sum I = 0$$


$$\sum I = I_1 + I_2 + I_3 - I_4 - I_5 = 0$$



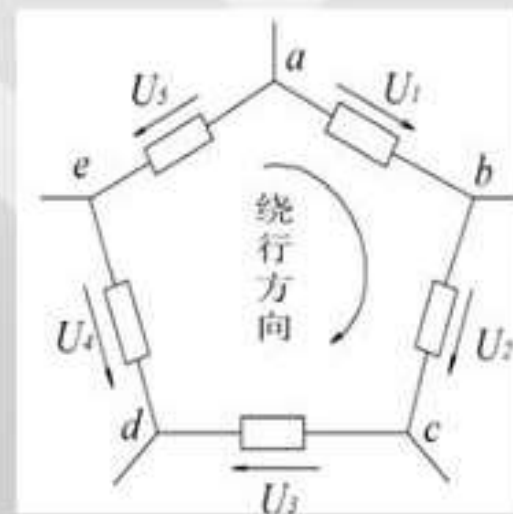2. 基尔霍夫电压定律 (KVL)

$$\sum U = 0$$

$$\sum U = U_1 + U_2 + U_3 - U_4 - U_5 = 0$$



Some Interesting experiments




lumped model

In the general circuit analysis, all the parameters of the circuit, such as impedance, capacitive reactance, inductive reactance are concentrated on each point in space, each component, and the signal between each point is transmitted instantaneously, this idealized circuit model is called a lumped circuit.

Generally speaking: An idealized circuit model

KCL:

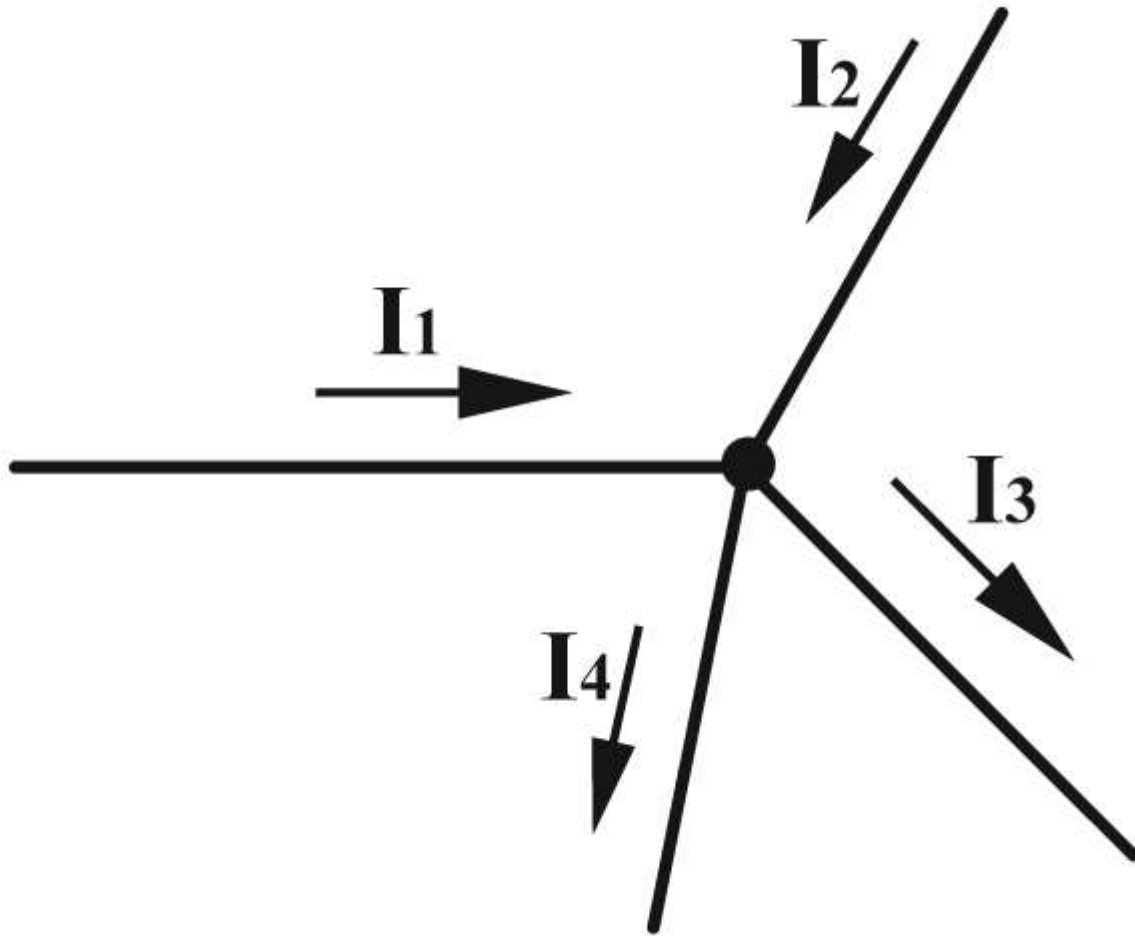


The total current of the incoming and outgoing circuit nodes is 0.

$$\sum u(t) = 0$$

例

取顺时针方向绕行：

$$\sum U = 0$$

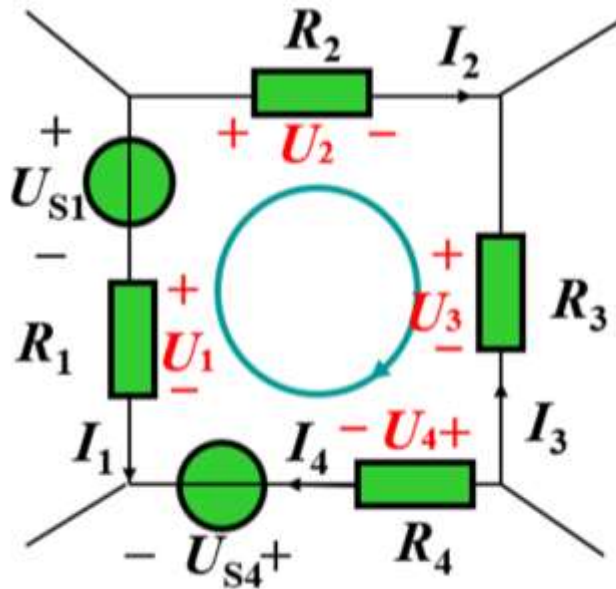

$$-U_1 - U_{S1} + U_2 + U_3 + U_4 + U_{S4} = 0$$


$$-U_1 + U_2 + U_3 + U_4 = U_{S1} - U_{S4}$$

$$\text{即 } \sum U_R = \sum U_S$$

电阻压降 电源压升

The algebraic sum of the potential difference (voltage) at both ends of all elements of the closed loop is equal to zero.


Principle of KCL and KVL

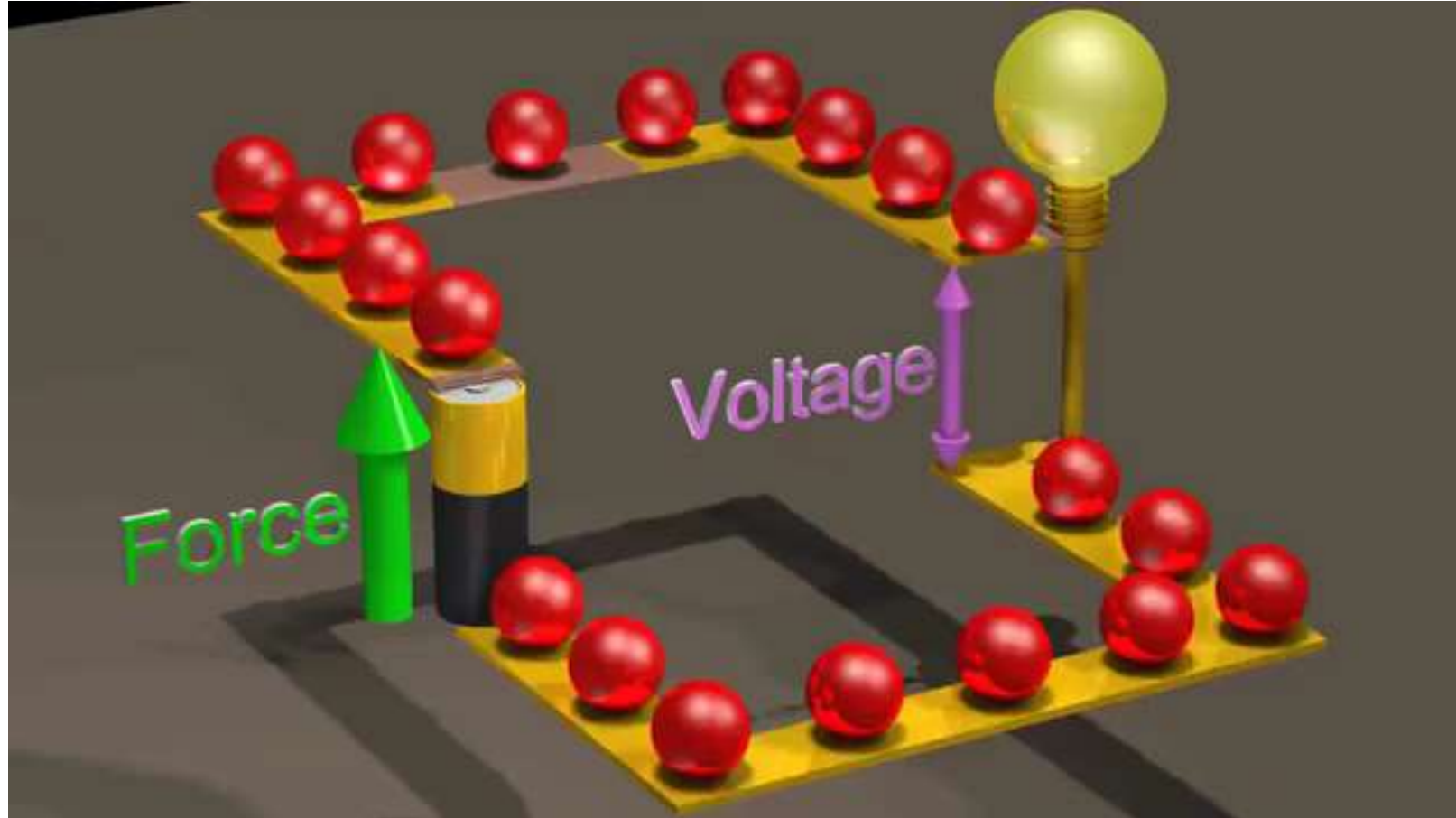


Discuss: Is Kirchhoff's law always true?



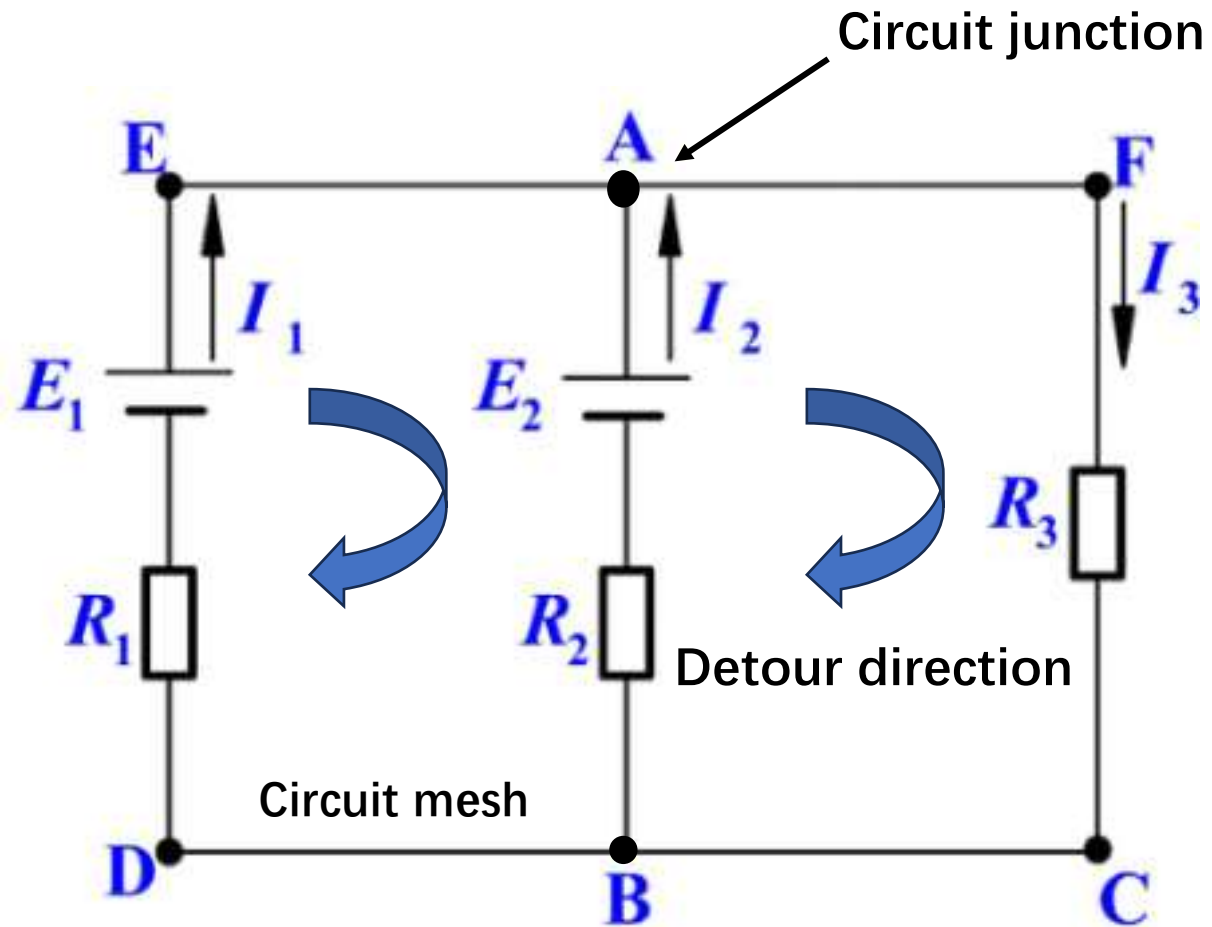
TEST: Misjudgment caused by testing equipment




$$V = I \cdot R$$

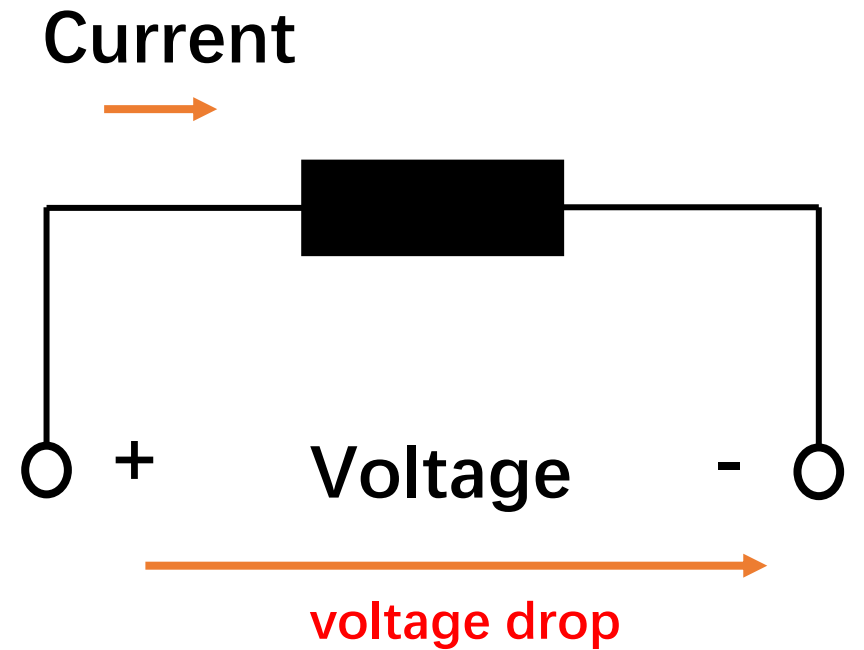

Question: I_1 I_2 I_3 ? & U ?

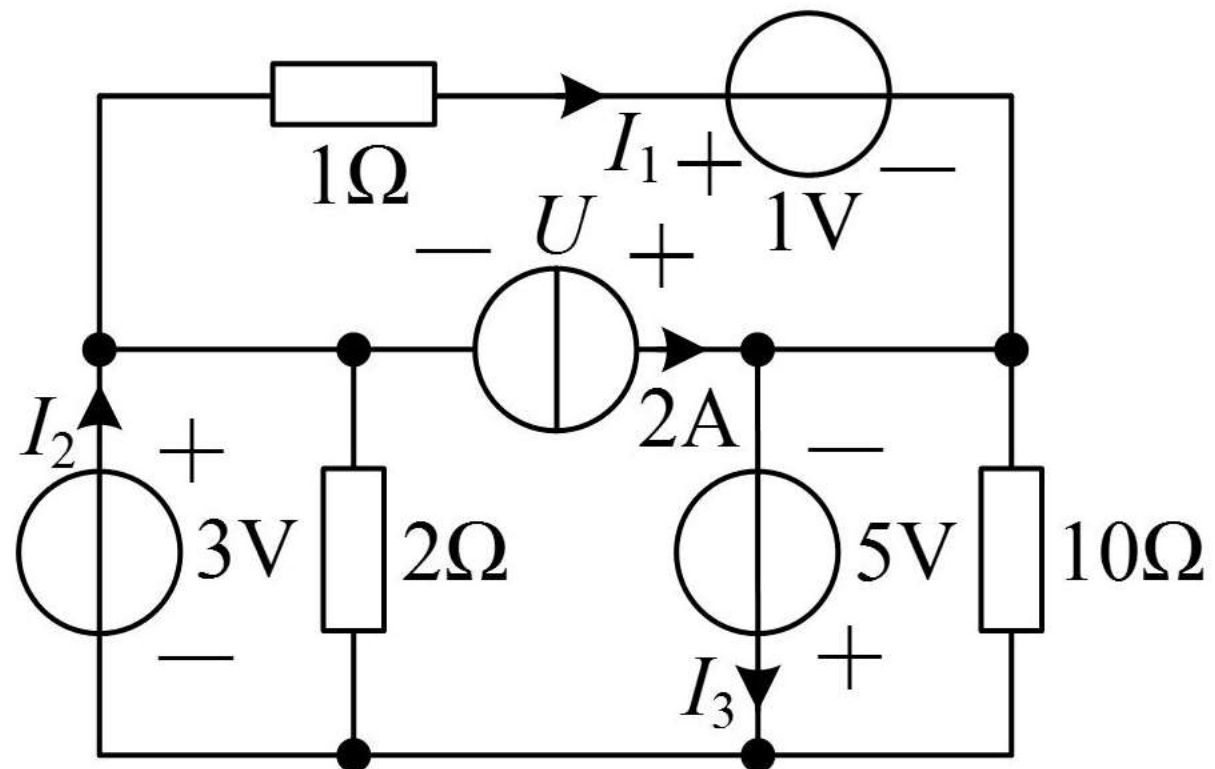


3 Thevenin-Norton theorem

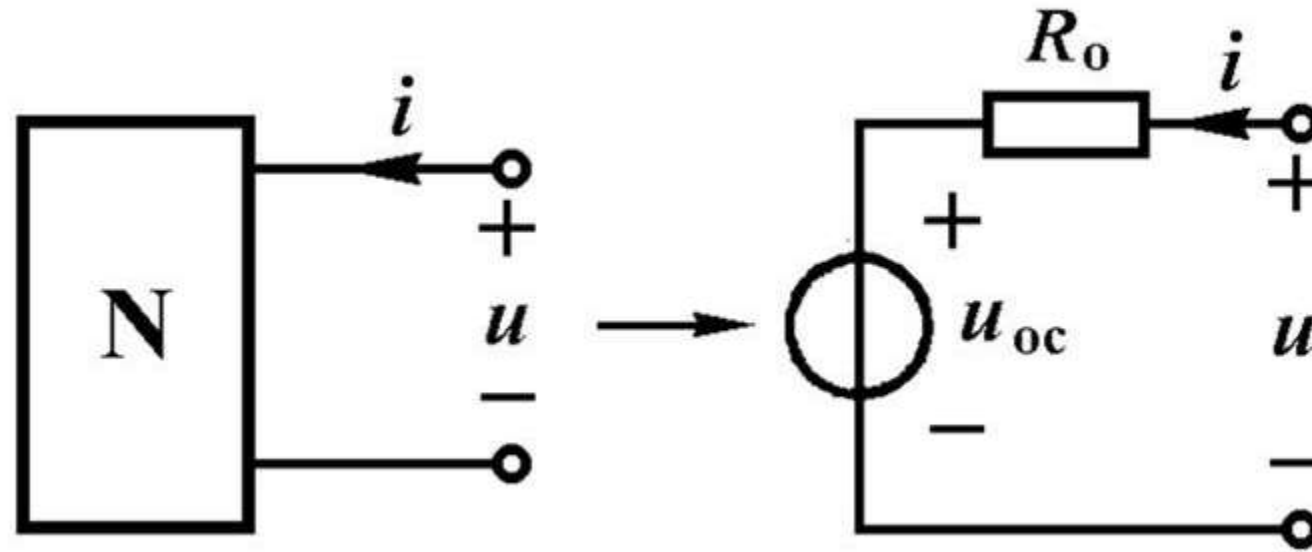


Both ends of a linear network consisting of an independent voltage source, an independent current source, and a resistance can be electrically equivalent by a combination of an independent voltage source and a series resistance.

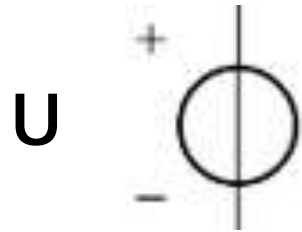Ideal Voltage source & Ideal Real Current source



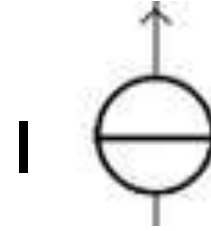Constant
Voltage
number &
Constant
Voltage
drop




Constant
Current
number &
Constant
Current
direction


Real Voltage source

&

Real Current source

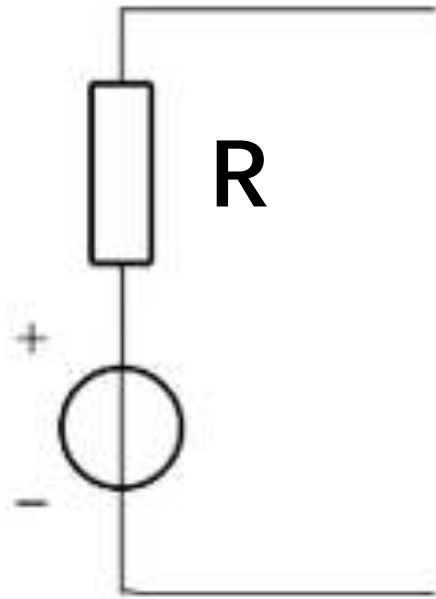

With a series resistance

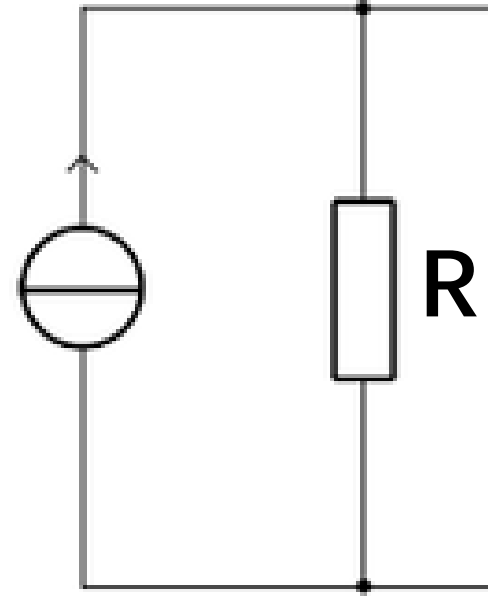

With a parallel resistance


Source transformation



The circuit structure is simplified


Real Voltage source \longleftrightarrow Real Current source

Equivalent !!!

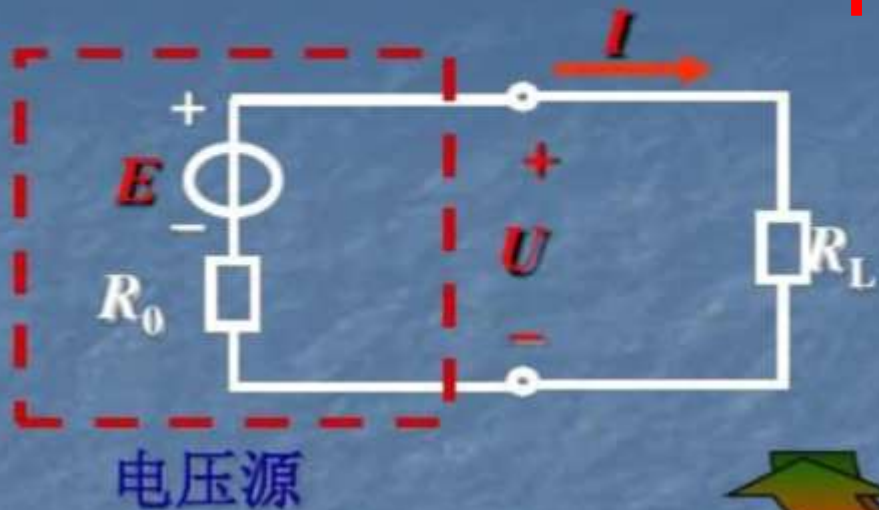

由图a:

$$U = E - IR_0$$

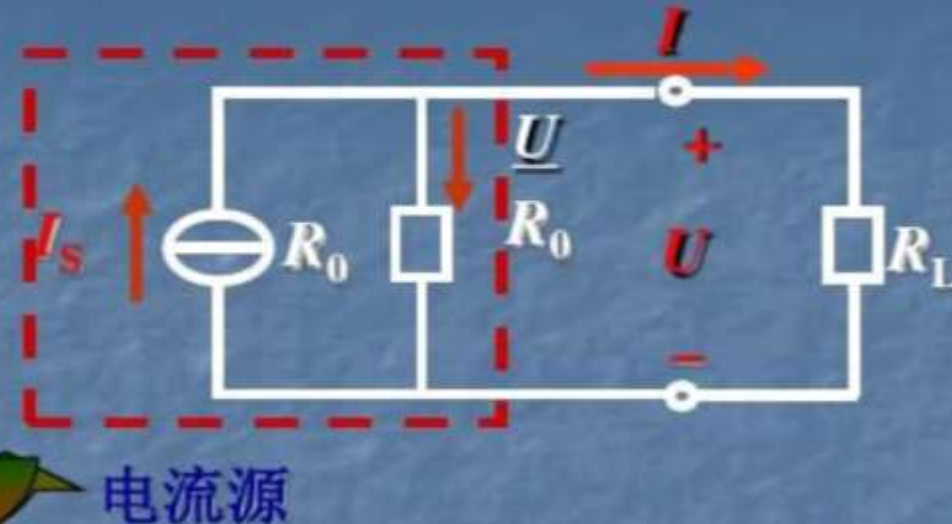


由图b:




$$U = I_s R_0 - IR_0$$

等效变换条件:

$$\begin{cases} E = I_s R_0 \\ I_s = \frac{E}{R_0} \end{cases}$$

Thevenin's law


 


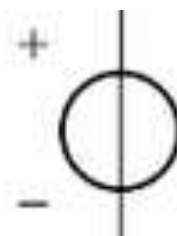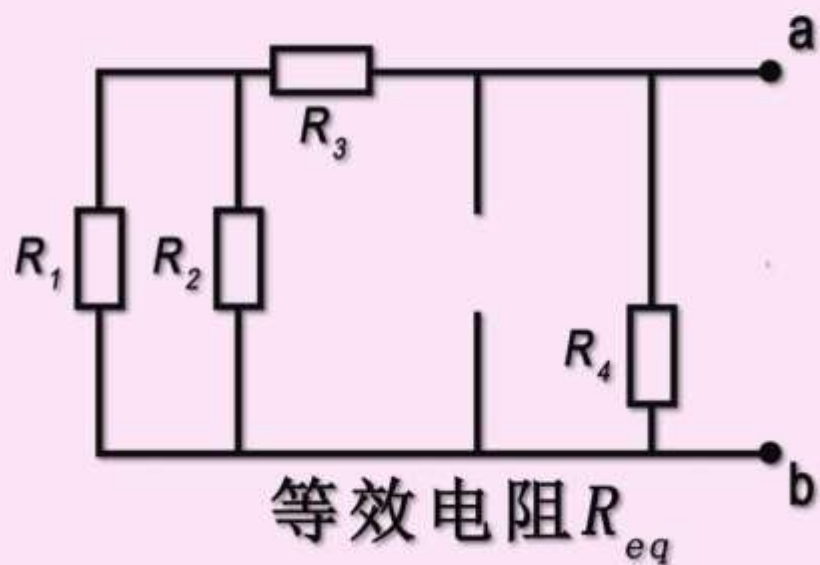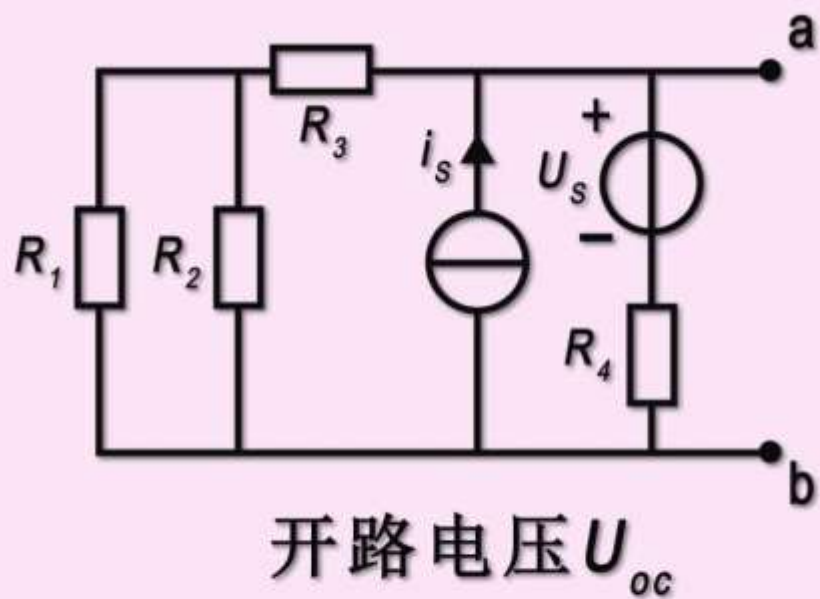

Switch On




Switch Off

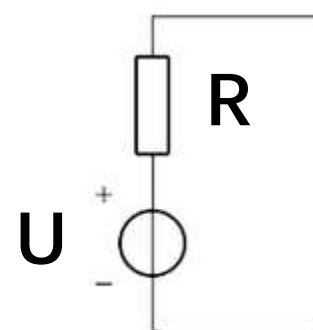
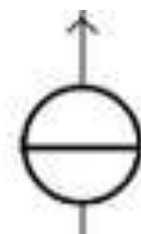


$$U = U_{ab} \quad R = R_{eq}$$

Norton's law

 


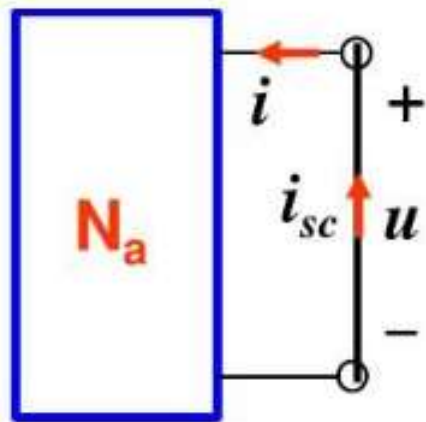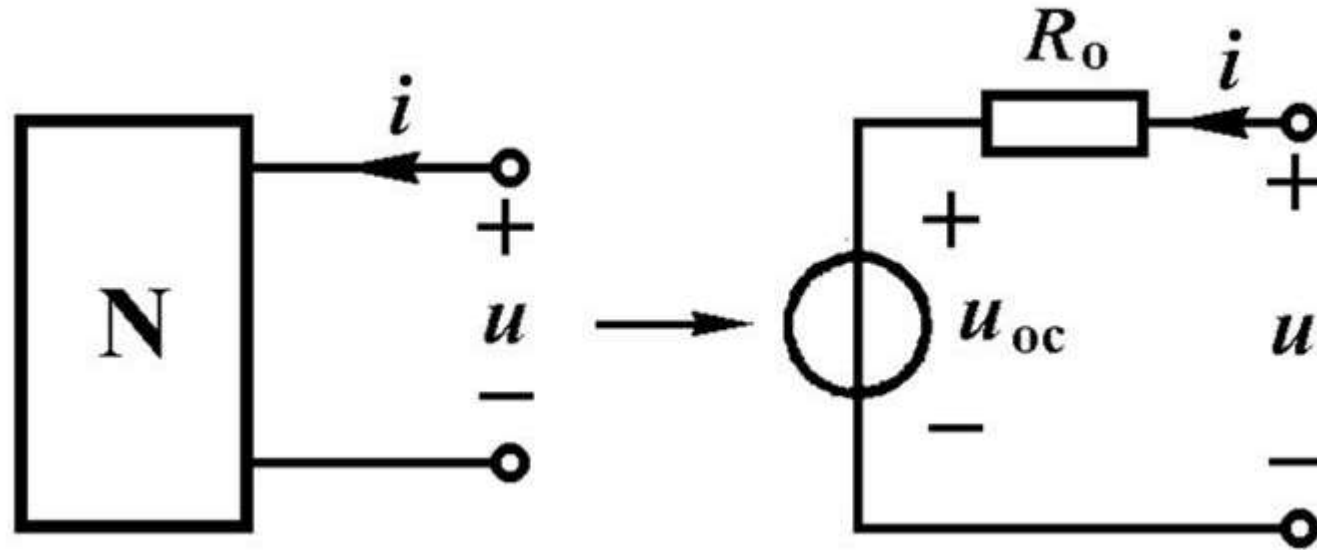Real Voltage source \longleftrightarrow Real Current source




$$i = i_{sc} + u/R_{eq}$$


\longleftrightarrow

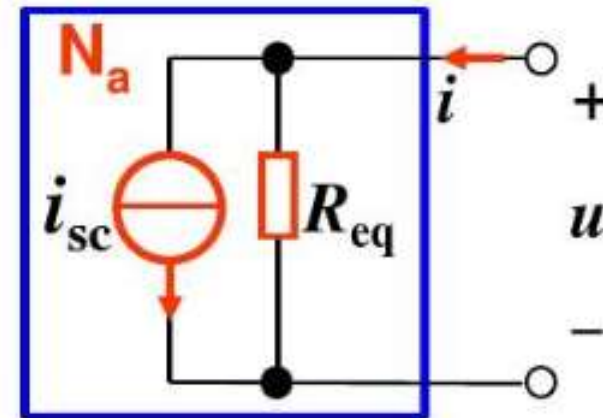

Some considerations:


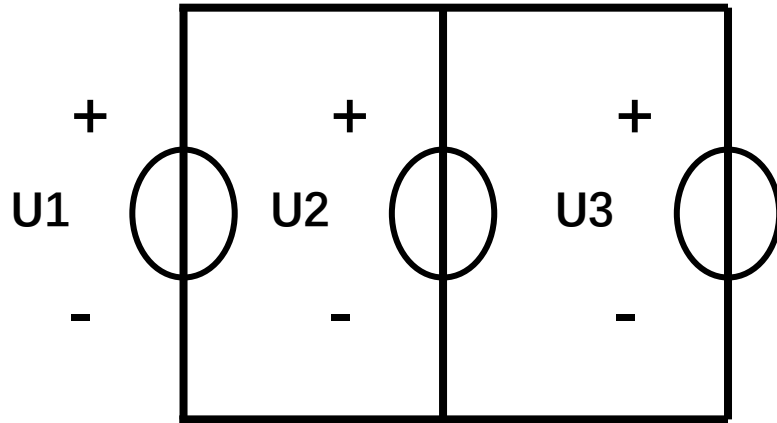


$U=???$

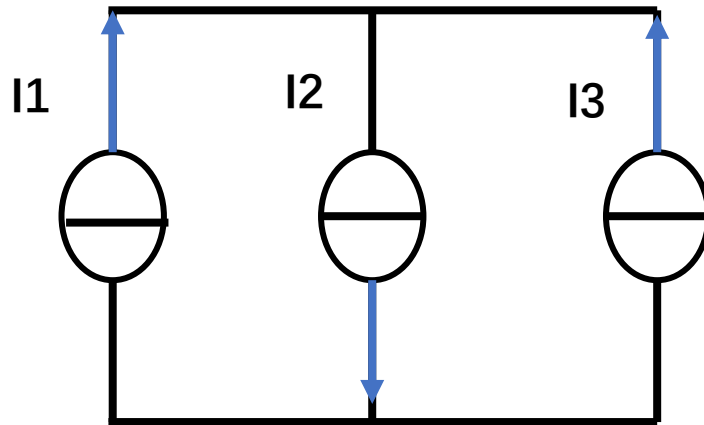

$I=???$

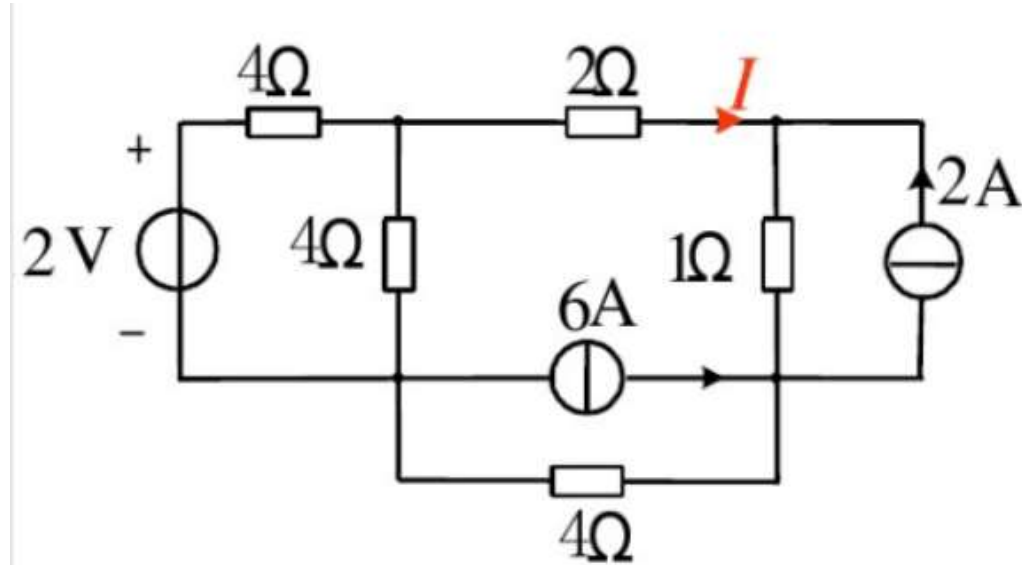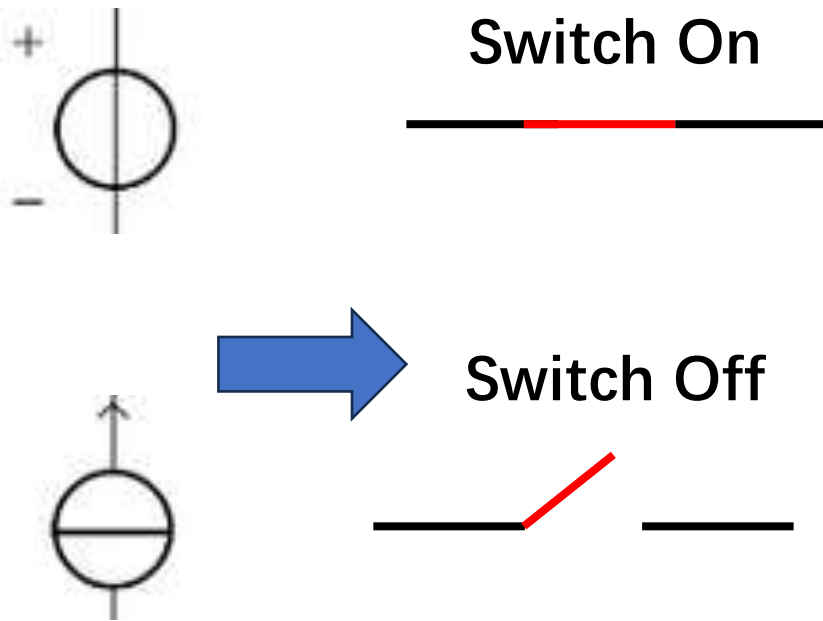Further application: Superposition Principle



The contribution of each power supply to the circuit can be considered separately!!!